

LAST IN FIRST OUT (STACK)

Nguyen Hong Nhat


Pham Dong Tra

Nguyen Nho Truong


Mentor: Khoa Le

ABSTRACT

What is LIFO ?

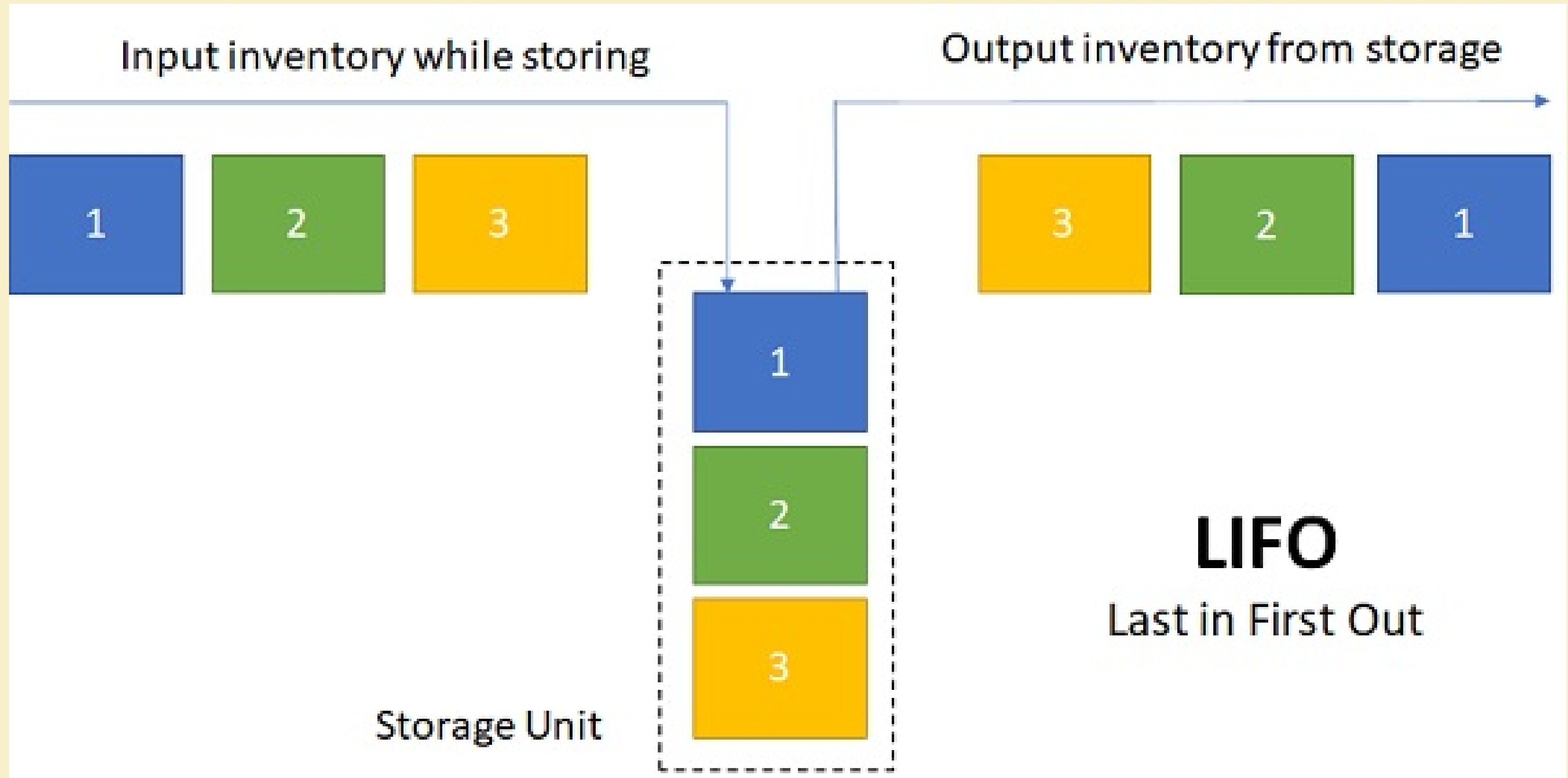


HIGH LEVEL BLOCK

 


Port	Size	Direction	Description
Clk	1	Input	System clock
rst	1	Input	Asynchronous reset, active LOW
wr	1	Input	Write enable signal (Push) to store data into the stack
rd	1	Input	Read enable signal (Pop) to retrieve data from the stack
data	3	Input	Parallel input data bus (3-bit width)
dataOut	3	Output	Parallel output data bus (3-bit width)
empty	1	Output	Status flag indicating the stack is currently empty
full	1	Output	Status flag indicating the stack is full
ud	1	Output	Underflow: Error flag triggered when attempting to read from an empty stack
ov	1	Output	Overflow: Error flag triggered when attempting to write to a full stack


EXPECTED WAVEFORM

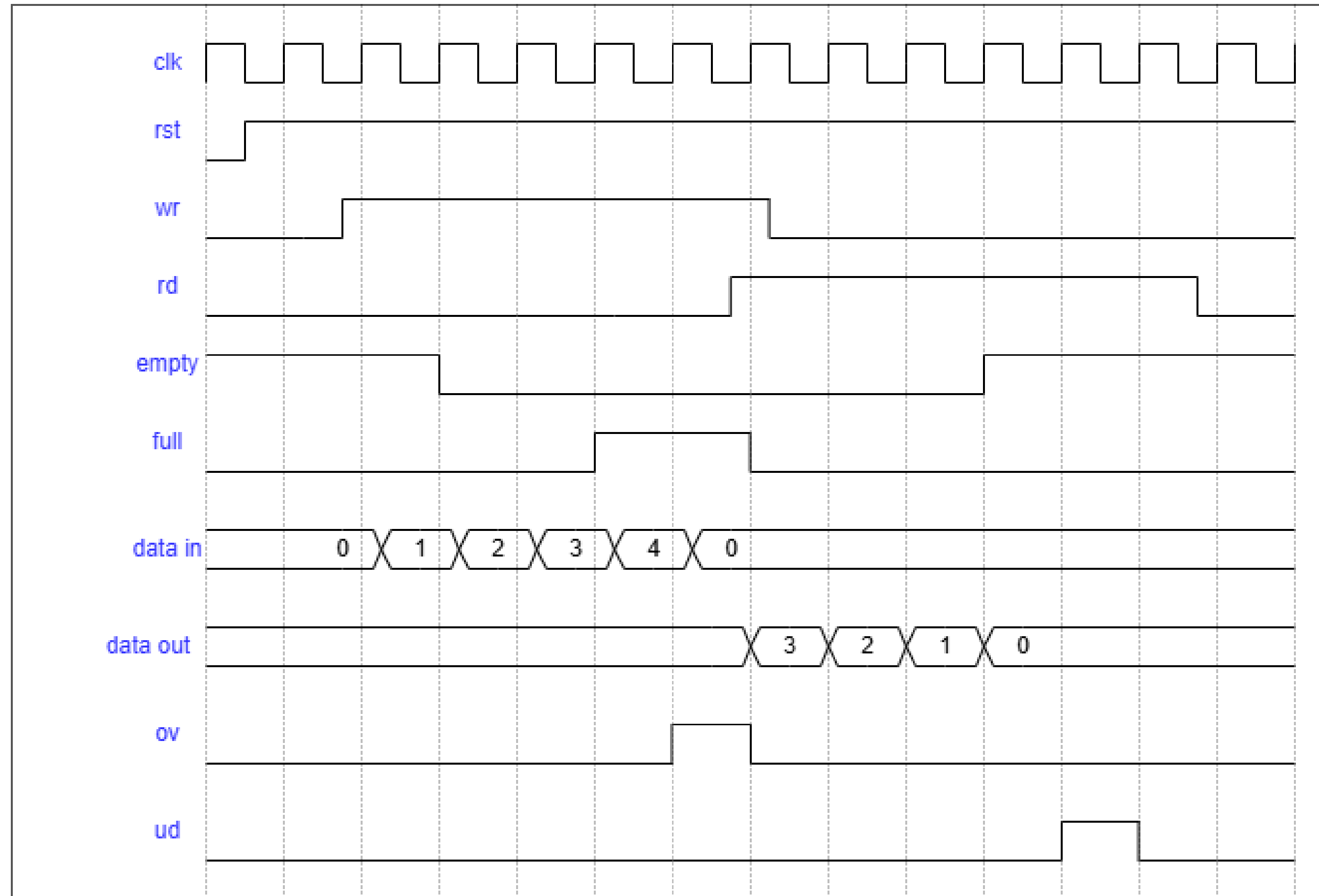


HIGH LEVEL BLOCK

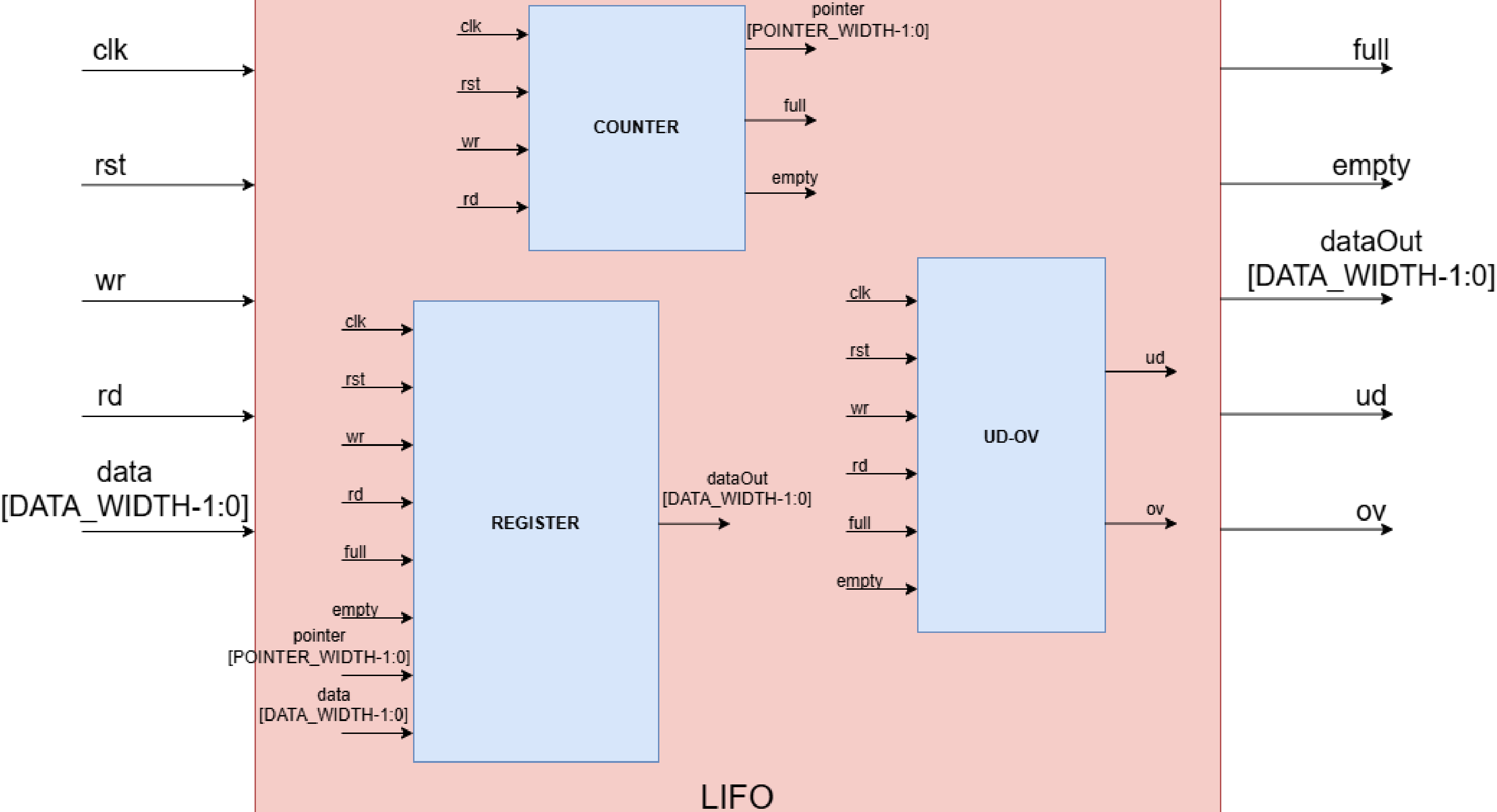


LOW LEVEL BLOCK controller

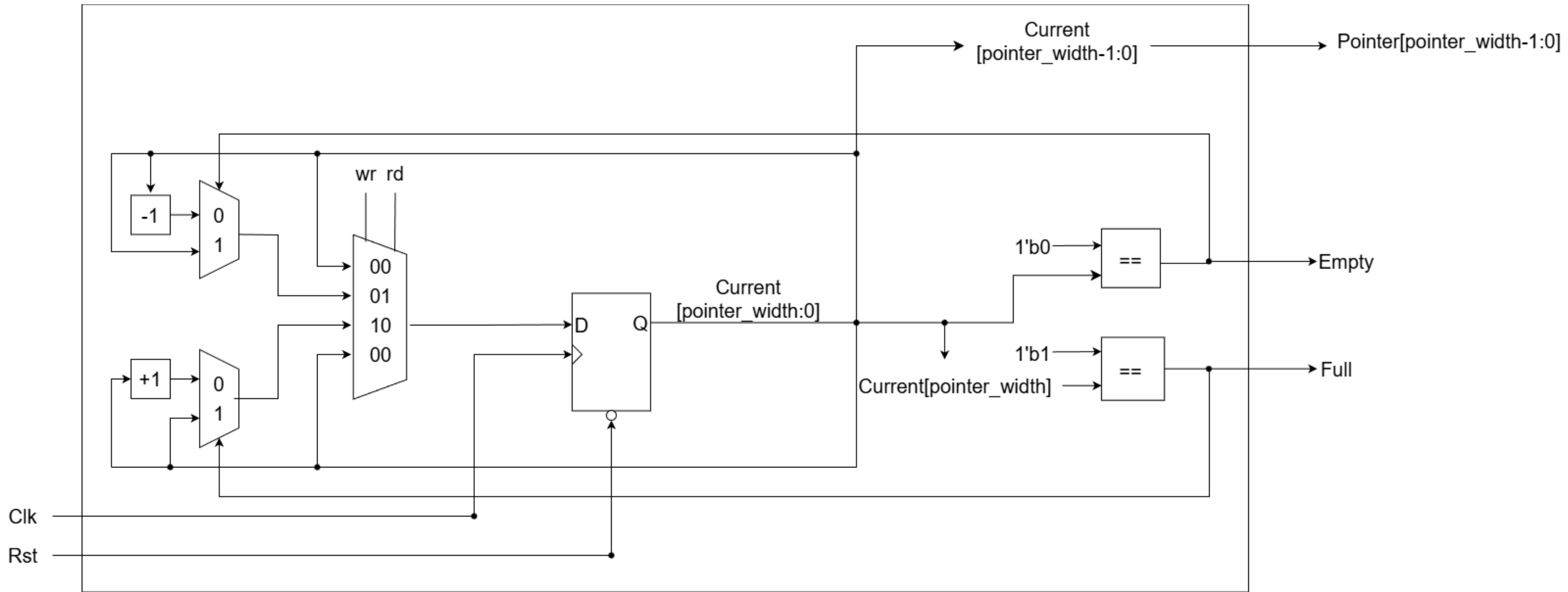


LOW LEVEL BLOCK
UD-OV

 

LOW LEVEL BLOCK Register

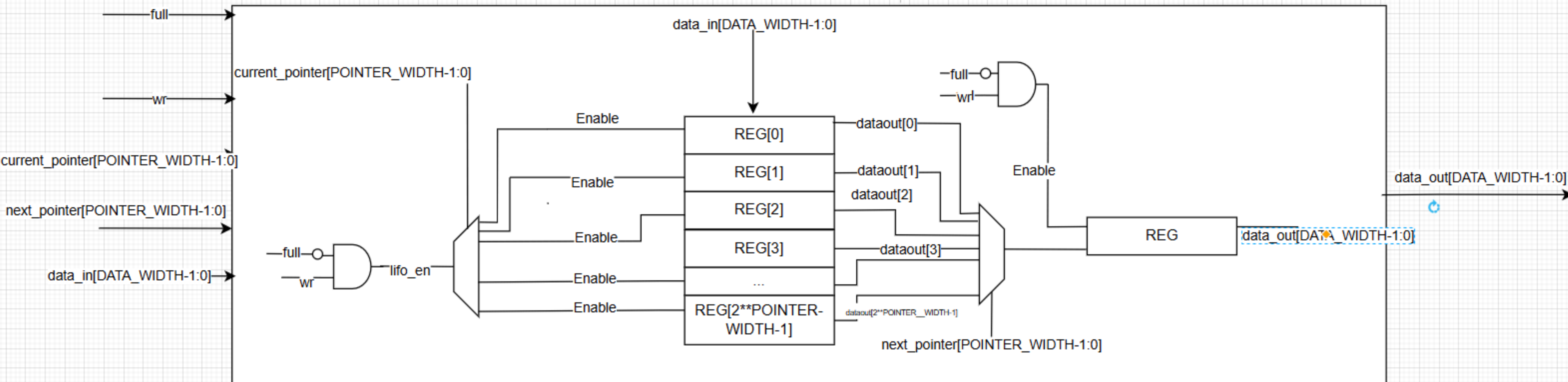

LOW LEVEL BLOCK REG

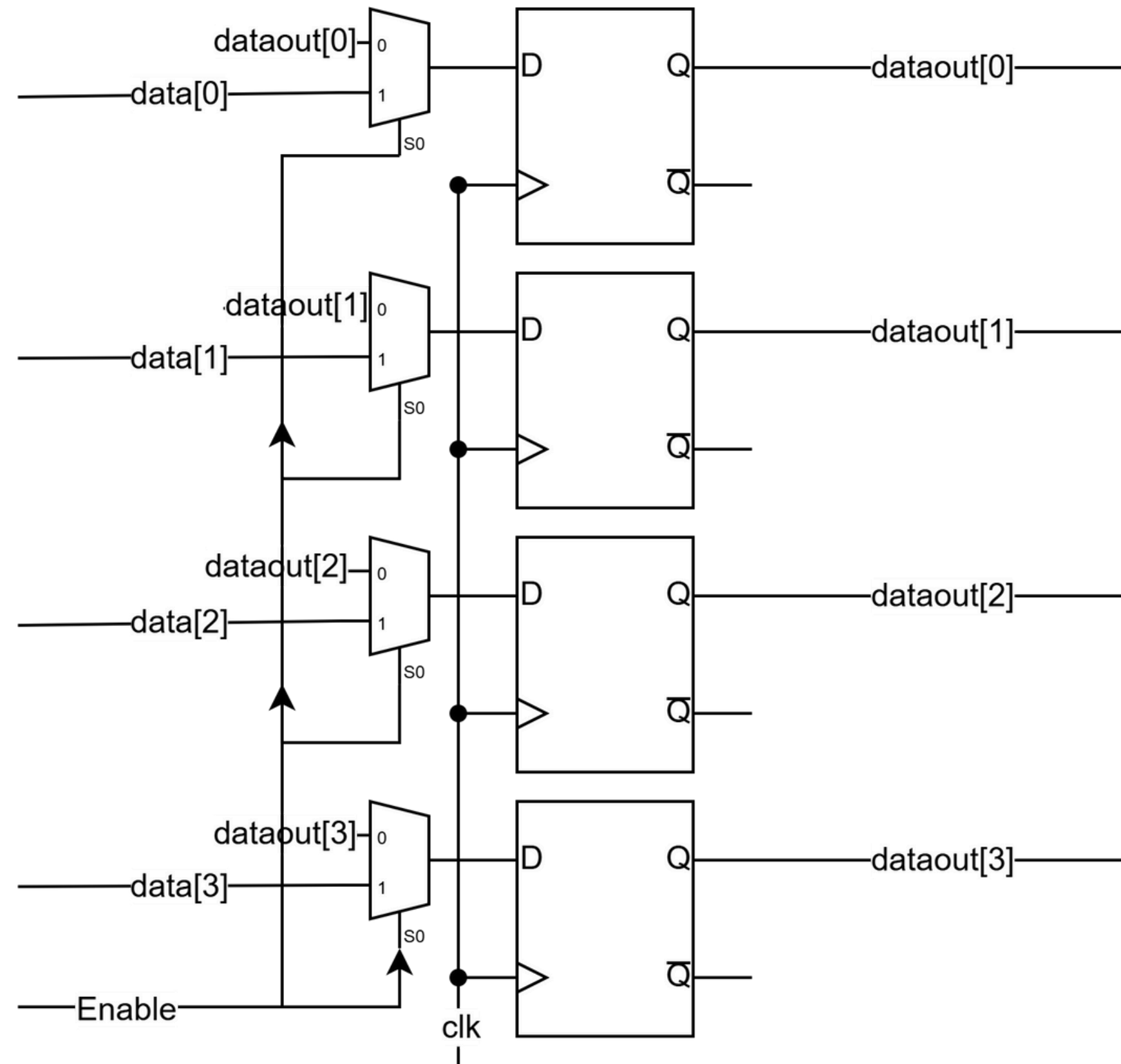

RTL DESCRIPTION

```
1 module counter#(  
2     parameter pointer_width = 2'd2  
3 )(  
4     input  clk,rst,wr,rd,  
5     output full, empty,  
6     output [pointer_width-1:0]pointer  
7 );  
8     reg [pointer_width:0] current;  
9     always @(posedge clk, negedge rst) begin  
10         if(!rst) current<=0;  
11         else begin  
12             case({wr,rd})  
13                 2'b00: current<=current;  
14                 2'b01: current<=(empty==0)? (current-1):current;  
15                 2'b10: current<=(full==0)?(current+1): current;  
16                 2'b11: current<=current;  
17                 default current<=current;  
18             endcase  
19         end  
20     end  
21     assign empty=(current==0)? 1'b1:0;  
22     assign full= (current[pointer_width]==1'b1) ? 1:0;  
23     assign pointer= current[pointer_width-1:0];  
24 endmodule
```

RTL DESCRIPTION

```
26 module OVUD(  
27     input empty,full,clk,rst,wr,rd,  
28     output reg ud,ov  
29 );  
30     always @(posedge clk,negedge rst) begin  
31         if(!rst) begin  
32             ud<=0;  
33             ov<=0;  
34         end  
35         else begin  
36             ud<=empty&rd;  
37             ov<=full&wr;  
38         end  
39     end  
40 endmodule
```


RTL DESCRIPTION

```
42 module register#(  
43     parameter pointer_width=2'd2,  
44     parameter data_width=2'd3  
45 )(  
46     input [pointer_width-1:0] pointer,  
47     input [data_width-1:0] data,  
48     input clk,wr,rd,rst,full,empty,  
49     output reg [data_width-1:0] dataOut  
50 );  
51     reg [data_width-1:0] ghi [(1<<pointer_width)-1:0];  
52     always @(posedge clk) begin  
53         if(wr&&!full) ghi[pointer]<=data;  
54     end  
55     always @(posedge clk, negedge rst) begin  
56         if( !rst) dataOut<=0;  
57         else if (rd&&!empty) dataOut<=ghi[pointer-1'b1];  
58         else dataOut<=dataOut;  
59     end  
60 endmodule
```

RTL DESCRIPTION

```
62 module LIFO#(  
63     parameter pointer_width=2'd2,  
64     parameter data_width=2'd3  
65 )(  
66     input clk,rst,wr,rd,  
67     input [data_width-1:0] data,  
68     output full, empty,  
69     output [data_width-1:0] dataOut,  
70     output ud,ov  
71 );  
72     wire [pointer_width-1:0] pointer;  
73     counter #(.pointer_width(pointer_width))  
khai1(.clk(clk),.rst(rst),.wr(wr),  
74         .rd(rd),.full(full),.empty(empty),.pointer(pointer));  
75     OVUD  
khai2(.clk(clk),.rst(rst),.wr(wr),.rd(rd),.full(full),.empty(empty),  
76         .ud(ud),.ov(ov));  
77     register #(.pointer_width(pointer_width),.data_width(data_width))  
78     khai3(.pointer(pointer),.data(data),.clk(clk),  
  
        .dataOut(dataOut),.wr(wr),.rd(rd),.rst(rst),.empty(empty),.full(full));  
79 endmodule
```

ACTUAL WAVEFORM

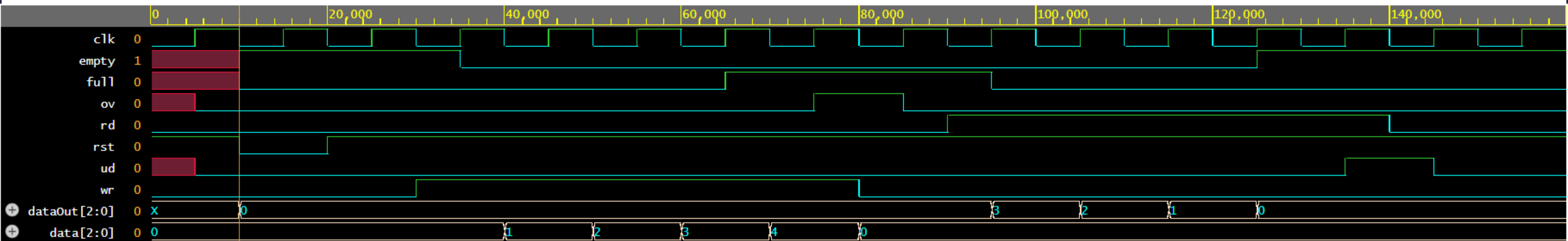

SYNTHESIS + STA

QOR

Timing			

Clock Period			

des_clk	500.0		
Cost Group	Critical Path Slack	TNS	Violating Paths

cg_enable_group_des_clk	67.2	0.0	0
default	No paths	0.0	
des_clk	No paths	0.0	
in2out	No paths	0.0	
in2reg	59.3	0.0	0
reg2out	60.4	0.0	0
reg2reg	213.0	0.0	0

Total		0.0	0
Instance Count			

Leaf Instance Count	338		
Physical Instance count	0		
Sequential Instance Count	161		
Combinational Instance Count	177		
Hierarchical Instance Count	18		
Area			

Cell Area	1204.182		
Physical Cell Area	0.000		
Total Cell Area (Cell+Physical)	1204.182		
Net Area	0.000		
Total Area (Cell+Physical+Net)	1204.182		

Power	

Leakage Power	128.445 nW
Dynamic Power	651442.199 nW
Total Power	651570.644 nW
Number of Clock Gating Logic	18
Max Fanout	20 (clk)
Min Fanout	0 (rst)
Average Fanout	2.5
Terms to net ratio	3.5014
Terms to instance ratio	3.6361
Runtime	11.052196 seconds
Elapsed Runtime	32 seconds
Genus peak memory usage	1609.55
Innovus peak memory usage	no_value
Hostname	dtvt05.taile60e1a.ts.net

Netlists

```
module RC_CG_MOD(enable, ck_in, ck_out, test);  
    input enable, ck_in, test;  
    output ck_out;  
    wire enable, ck_in, test;  
    wire ck_out;  
    TLATNTSCAX2 RC_CGIC_INST(.E (enable), .CK (ck_in), .SE (test), .ECK (ck_out));  
endmodule
```

```
module RC_CG_MOD_1(enable, ck_in, ck_out, test);  
    input enable, ck_in, test;  
    output ck_out;  
    wire enable, ck_in, test;  
    wire ck_out;  
    TLATNTSCAX2 RC_CGIC_INST(.E (enable), .CK (ck_in), .SE (test), .ECK (ck_out));  
endmodule
```

```
module RC_CG_MOD_2(enable, ck_in, ck_out, test);  
    input enable, ck_in, test;  
    output ck_out;  
    wire enable, ck_in, test;  
    wire ck_out;  
    TLATNTSCAX2 RC_CGIC_INST(.E (enable), .CK (ck_in), .SE (test), .ECK (ck_out));  
endmodule
```

```
module RC_CG_MOD_3(enable, ck_in, ck_out, test);  
    input enable, ck_in, test;  
    output ck_out;  
    wire enable, ck_in, test;  
    wire ck_out;  
    TLATNTSCAX2 RC_CGIC_INST(.E (enable), .CK (ck_in), .SE (test), .ECK (ck_out));  
endmodule
```

```
module RC_CG_MOD_4(enable, ck_in, ck_out, test);  
    input enable, ck_in, test;  
    output ck_out;  
    wire enable, ck_in, test;  
    wire ck_out;  
    TLATNTSCAX2 RC_CGIC_INST(.E (enable), .CK (ck_in), .SE (test), .ECK (ck_out));  
endmodule
```